



## Introduction to Digital Design

Week 7: Clock, Latches, and Flip-Flops

Yao Zheng  
Assistant Professor  
University of Hawaii at Mānoa  
Department of Electrical Engineering


## Overview

- Sequential circuit
  - Output depends not just on present inputs but on past sequence of inputs.
- SR Latch
  - Feedback circuit for bit storage.
  - Race condition and level-sensitive latch.
- D Latch and D Flip-Flop
  - D Latch: inserted inverter ensures R always opposite of S
  - D Flip-Flop: bit storage that stores on clock edge.
- Clock signal
  - Flip-flop to generates periodic pulsing signal.
- Basic register

2
 
## Introduction

- Sequential circuit
  - Output depends not just on present inputs (as in combinational circuit), but on past sequence of inputs
    - Stores bits, also known as having "state"
  - Simple example: a circuit that counts up in binary
- This chapter will:
  - Design a new building block, a **flip-flop**, to store one bit
  - Combine flip-flops to build multi-bit storage – **register**
  - Describe sequential behavior with **finite state machines**
  - Convert a finite state machine to a **controller** – sequential circuit with a register and combinational logic



3.1

Note: Slides with animation are denoted with a small red "A" near the animated items

3


## Storing One Bit – Flip-Flops Example Requiring Bit Storage

- Flight attendant call button
  - Press call: light turns on
    - Stays on** after button released
  - Press cancel: light turns off
    - Stays off** after button released
  - Logic gate circuit to implement this?



Doesn't work.  $Q=1$  when  $Call=1$ , but doesn't stay 1 when  $Call$  returns to 0

 Need some form of "feedback" in the circuit




3.2

4
 
## First attempt at Bit Storage


- Need some sort of feedback
  - Does circuit on the right do what we want?
    - No: Once  $Q$  becomes 1 (when  $S=1$ ),  $Q$  stays 1 forever – no value of  $S$  can bring  $Q$  back to 0



5
 
## Bit Storage Using an SR Latch


- Does the circuit to the right, with cross-coupled NOR gates, do what we want?
  - Yes! How did someone come up with that circuit? Maybe just trial and error, a bit of insight...



6
 
### Example Using SR Latch for Bit Storage


- SR latch can serve as bit storage in previous example of flight-attendant call button
  - Call=1 : sets Q to 1
    - Q stays 1 even after Call=0
  - Cancel=1 : resets Q to 0
- But, there's a problem...




7

### Problem with SR Latch

 - Problem
  - If  $S=1$  and  $R=1$  simultaneously, we don't know what value Q will take



 
Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which. Known as a *race condition*.



8
 
### Problem with SR Latch


- Designer might try to avoid problem using external circuit
  - Circuit should prevent SR from ever being 11
  - But 11 can occur due to different path delays




9
 
### Problem with SR Latch

- Glitch can also cause undesired set or reset




Suppose this wire has 4 ns delay

 

10
 
### Solution: Level-Sensitive SR Latch


- Add enable input "C"
- Only let S and R change when  $C=0$ 
  - Ensure circuit in front of SR never sets  $SR=11$ , except briefly due to path delays
  - Set  $C=1$  after time for S and R to be stable
  - When C becomes 1, the stable S and R value passes through the two AND gates to the SR latch's S1 R1 inputs.



11
 
### Level-Sensitive D Latch

- SR latch requires careful design to ensure  $SR=11$  never occurs
- D latch relieves designer of that burden
  - Inserted inverter ensures R always opposite of S




D latch symbol

12

 
### Problem with Level-Sensitive D Latch

- D latch still has problem (as does SR latch)
  - When  $C=1$ , through how many latches will a signal travel?
  - Depends on how long  $C=1$ 
    - Clk\_A – signal may travel through multiple latches
    - Clk\_B – signal may travel through fewer latches



13

### Problem with Level-Sensitive D Latch

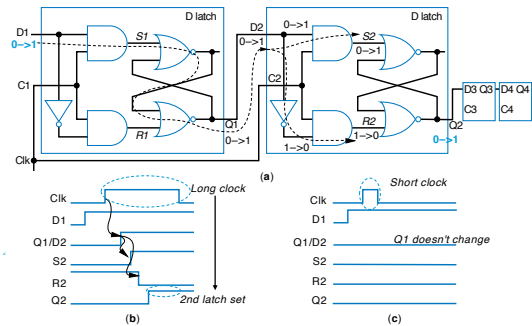


14

### D Flip-Flop

- Can we design bit storage that only stores a value on the rising edge of a clock signal?
- Flip-flop:** Bit storage that stores on clock edge

rising edges  
clk

 
- One design – master-servant
  - $\text{Clk} = 0$  – master enabled, loads D, appears at Qm. Servant disabled.
  - $\text{Clk} = 1$  – Master disabled, Qm stays same. Servant latch enabled, loads Qm, appears at Qs.
  - Thus, value at D (and hence at Qm) when Clk changes from 0 to 1 gets stored into servant



15

 
### D Flip-Flop

- Solves problem of not knowing through how many latches a signal travels when  $C=1$ 
  - In figure below, signal travels through exactly one flip-flop, for Clk\_A or Clk\_B
  - Why? Because on rising edge of Clk, all four flip-flops are loaded simultaneously – then all four no longer pay attention to their input, until the next rising edge. Doesn't matter how long Clk is 1.



16


### D Flip-Flop

 

17
 
### D Latch vs. D Flip-Flop


- Latch is level-sensitive
  - Stores D when  $C=1$
- Flip-flop is edge triggered
  - Stores D when C changes from 0 to 1
- Saying "level-sensitive latch" or "edge-triggered flip-flop" is redundant
- Comparing behavior of latch and flip-flop:



18
 
## Clock Signal

- Flip-flop Clk inputs typically connect to one clock signal
  - Coming from an oscillator component
  - Generates periodic pulsing signal
    - Below: "Period" = 20 ns, "Frequency" =  $1/20 \text{ ns} = 50 \text{ MHz}$
    - "Cycle" is duration of 1 period (20 ns); below shows 3.5 cycles



Period/Freq shortcut: Remember  $1 \text{ ns} \rightarrow 1 \text{ GHz}$

Freq.	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

19

## Flight-Attendant Call Button Using D Flip-Flop

- D flip-flop will store bit
- Inputs are Call, Cancel, and present value of D flip-flop, Q
- Truth table shown below



Call	Cancel	Q	D
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Preserve value: if  $Q=0$ , make  $D=0$ ; if  $Q=1$ , make  $D=1$

Cancel -- make  $D=0$

Call -- make  $D=1$

  
Let's give priority to Call -- make  $D=1$



Circuit derived from truth table, using Chapter 2 combinational logic design process

20

## Bit Storage Summary

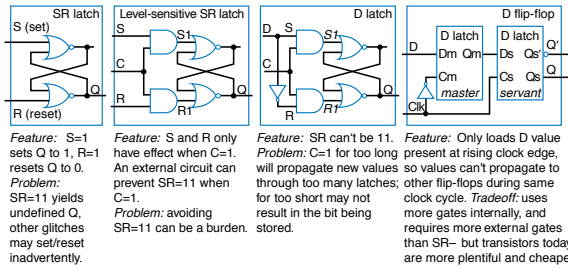


- We considered increasingly better bit storage until we arrived at the robust D flip-flop bit storage

21
 
## Basic Register


- Typically, we store multi-bit items
  - e.g., storing a 4-bit binary number
- Register:** multiple flip-flops sharing clock signal
  - From this point, we'll use registers for bit storage
    - No need to think of latches or flip-flops
    - But now you know what's inside a register



22
 
## Example Using Registers: Temperature Display


- Temperature history display
  - Sensor outputs temperature as 5-bit binary number
  - Timer pulses C every hour
  - Record temperature on each pulse, display last three recorded values



23

## Example Using Registers: Temperature Display

- Use three 5-bit registers

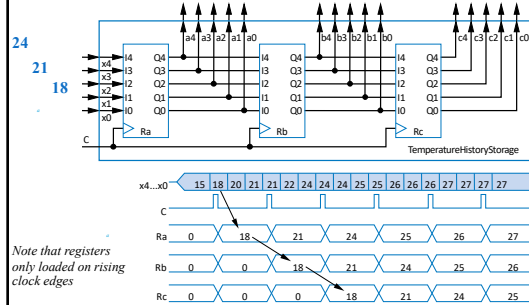

Note that registers only loaded on rising clock edges

24

### Summary

- Sequential circuit
  - Output depends not just on present inputs but on past sequence of inputs.
- SR Latch
  - Feedback circuit for bit storage.
  - Race condition and level-sensitive latch.
- D Latch and D Flip-Flop
  - D Latch: inserted inverter ensures R always opposite of S
  - D Flip-Flop: bit storage that stores on clock edge.
- Clock signal
  - Flip-flop to generates periodic pulsing signal.
- Basic register

25